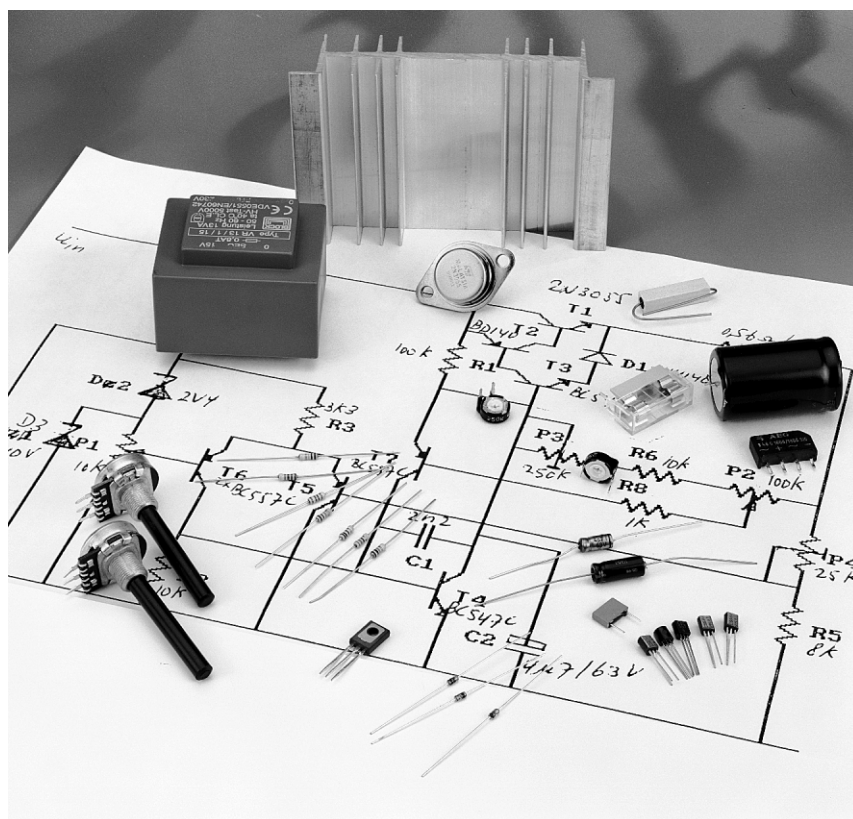


# general purpose variable power supply

*easily adapted to individual requirements*

A variable power supply is described that in spite of its simple design has two clear benefits. In the first place, it is built from discrete, readily available components, and in the second place, it can be readily adapted to individual requirements. Rules of thumb to do this are included in the article.



## INTRODUCTION

The power supply is designed along fairly traditional lines, resulting in a unit whose output voltage as well as its current limiting is variable. In principle, both can be varied from nought, but in this design it was decided to make the peak values of voltage and current variable. These peak values can be varied from 10 V to 40 V and from 500 mA to 2.5 A. This makes the supply suitable for use in a variety of applications.

## CIRCUIT DESCRIPTION

Although the supply does not contain a single integrated circuit, it is still very compact.

The circuit diagram in **Figure 1** deals merely with the regulator sec-

tion, since the ratings of transformers, bridge rectifier and smoothing capacitors depend on the required output voltage and current.

The regulator proper is transistor  $T_1$  in series with input and output terminals. In conjunction with transistors  $T_2$  and  $T_3$ , it forms an emitter follower that has good current amplification and a low base-emitter potential.

The differential amplifier formed by  $T_5$  and  $T_6$  compares the voltage at the wiper of  $P_1$  with a part of the output voltage derived from potential divider  $R_5$ - $P_4$ . The amplifier tends to equalize these voltages by varying the drive to the emitter follower via  $T_4$ . When the output voltage exceeds the value set

Transistor  $T_7$  provides the requisite current limiting, for which  $R_4$  functions as the current sensor. When the current through, and therefore the voltage across, this resistor exceeds a certain level, the potential across network  $P_3$ - $R_6$ - $P_2$  increases to a value that causes  $T_7$  to conduct harder (owing to the potential at the base of  $T_2$ ). The resulting higher current into the base of  $T_4$  causes this transistor to reduce the base voltage of  $T_3$ . The emitter follower then conducts less hard, whereupon the output voltage drops. Since the current through  $T_3$  and  $D_1$  is small, there is hardly any heat dissipation and the current limiting is virtually immune to temperature drift.

Summarizing the action of the potentiometers:  $P_1$  enables the output voltage to be set between 0 V and maximum.

Potentiometer  $P_4$  sets the peak output voltages according to

$$U_{\max} = 10(1 + P_4/R_5) \quad [\text{V}]$$


where the values of  $P_4$  and  $R_5$  are in  $k\Omega$ . When  $P_4 = 0$  (wiper at  $U_{out}$ ), the peak output voltage is 10 V, and when  $P_4 = 25 k\Omega$ ,  $U_{max} = 40$  V.

Potentiometer  $P_2$  enables the output current to be set between 0 A and a peak value determined by the setting of  $P_3$ . With  $P_3 = 0$  (wiper at  $R_6$ ), the peak output current is 2.5 A and with  $P_3 = 250\text{ k}\Omega$ , the peak current is about 500 mA.

## A PRACTICAL CASE

The rating of the transformer, bridge rectifier and electrolytic smoothing capacitor to precede the regulator is determined on the basis of the circuit in **Figure 2**.

Assume that an output voltage variable between 0 V and 18 V, and the current limiting variable between 0 A and 1 A, is required. This requires a mains transformer rated at not less than 18 V a.c. and an output current of not less than  $\sqrt{2} \times 1 = 1.4$  A. Furthermore, losses in the bridge rectifier, series transistor ( $T_1$ ) and resistor  $R_4$  must be taken into account. This is why it is better to use the rule of thumb that the transformer

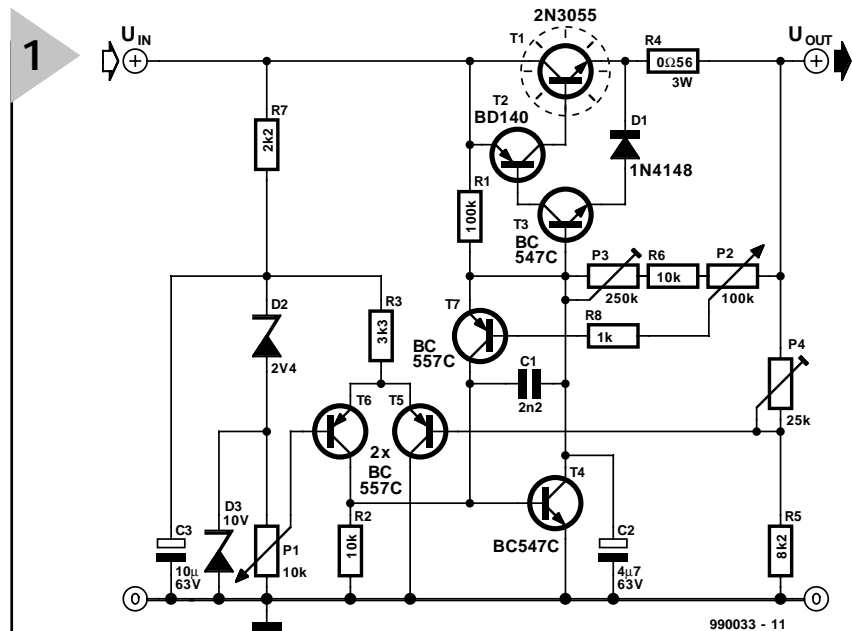

**Figure 1. Circuit diagram of the regulator section of the power supply unit.**

rating should be about 50 per cent higher than the theoretically needed power: in this case, a secondary alternating voltage of 18 V and a rating of 27 VA.

By rule of thumb, the bridge rectifier should also be rated about 50 per cent higher than theoretically required. This means that the requisite one should be a 35 V/1.5 A type.

The value of smoothing capacitor  $C$  determines the minimum input voltage to the regulator. Since the wanted output voltage is 18 V, and the potential drop across  $R_4$  with an output current of 1 A is 0.56 V, and the drop across  $T_1$  is about 3 V, the minimum input voltage is 21.6 V.

## The transformer


provides, after rectification and smoothing, a voltage of  $\sqrt{2} \times 18 = 25.4$  V. This

should be reduced by about 1.4 V to account for losses in the bridge rectifier, but in practice these losses are compensated by the fact that most transformers provide a higher voltage than nominal.

The maximum permitted ripple voltage is the difference between the available direct voltage and the requisite input voltage, that is, 3.8 V.

The value of  $C$  in microfarad is calculated with the formula  $C = IT/U_r$ , where  $I$  is the peak output current in A,  $T$  is the period after full-wave rectification (0.01 s), and  $U_r$  is the ripple voltage in V. Substituting the values found earlier

**Figure 2. Circuit diagram of the power section: the values and ratings of the components depend on individual requirement.**

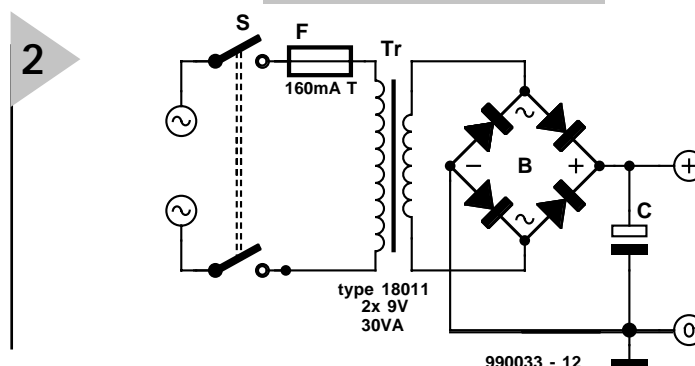

gives:

$$C = 1 \times 0.01 / 3.8 = 2632 \text{ } [\mu\text{F}]$$

Bearing in mind the drop across the bridge rectifier, this value should be rounded upward to, say, 3300  $\mu\text{F}$ . The operating voltage should 35 V. There may be situations where a value of 3300  $\mu\text{F}$  is not easily obtained, and a 4700  $\mu\text{F}$  type should then be used.

It is advisable to precede the mains transformer by a mains fuse. This should be rated at  $1.25I_{\text{max}}$ , that is in this case:

$$1.25 \times 27 / 230 = 147 \text{ mA,}$$

which is rounded upward to 150 mA (T is slow-blow).

### HEAT SINK

Finally, the rating and size of a suitable heat sink must be determined. Again, this may be done with the aid of rule of thumb.

The maximum dissipation of the series transistor is the product of the input voltage and the maximum output current. In this case, this is

$$26 \times 1 = 26 \text{ W.}$$

It will be assumed that the case tem-

perature of the transistor should not rise above 70 °C. The inner junction will, of course, get hotter (in the case of an 2N3055 about 105 °C), but this does not matter, because the transistor is capable of withstanding 120–150 °C.

The heat sink temperature of 70 °C is about 50 °C higher than the average room temperature. This means that there is 50 K ( $K = ^\circ\text{C}$ ) available to dissipate 26 W. This means that the thermal resistance of the heat sink should be  $50 / 26 = 1.9 \text{ K W}^{-1}$ .

When a heat sink of this rating is used, the power supply can provide an output voltage of 1 V and an output current of 1 A for hours without any problems whatsoever. If it is assumed that this extreme situation will never arise and that  $T_1$  may on occasion get hotter than 70 °C, a heat sink with a thermal resistance of  $3 \text{ K W}^{-1}$  may be used. Bear in mind that isolation washers between transistor and heat sink increase the thermal resistance by  $0.2\text{--}0.9 \text{ K W}^{-1}$ , depending on the material of the washer.

It should be noted that a heat sink at 70 °C can singe your skin badly and it should therefore never be touched with bare hands.

### ADDITIONAL NOTES

Although the regulator circuit can be

used for many requirements, the input voltage to it should not drop below 15 V to ensure that zener diodes  $D_2$  and  $D_3$  continue to function correctly.

Also, it is advisable to insert a fuse between the smoothing capacitor and the regulator. Its rating should be equal to, or slightly higher than, the peak output current.

To ensure the requisite stability, an electrolytic capacitor with a value of about 1/10 of that of the smoothing capacitor should be added across the output terminals.

### SETTING UP

When the unit has been completed and checked thoroughly, connect a voltmeter (50 V d.c. range) to the output terminals, turn  $P_1$  fully clockwise (maximum), and adjust  $P_4$  until the voltmeter shows the wanted output voltage (for instance, as in the foregoing example, to 18 V).

Terminate the output by a 24 V, 50 W load (a halogen light bulb is ideal for this) in series with an ammeter (set to 10 A). Turn  $P_3$  fully clockwise (lowest current), adjust  $P_2$  for maximum current, and set  $P_3$  for the wanted maximum current.

[990033]